

1. Open the Loop: Insert a 0V voltage source in the feedback path. A good technique is to insert it between the output and the feedback network to avoid changing the DC operating point.
2. Add Stimulus: Configure the inserted voltage source with an AC amplitude of 1 in the “Advanced” tab of the component properties.
3. Ensure Proper Biasing: Use a large capacitor (e.g. 1kF) in series with a large inductor (e.g. 1kH) to inject the AC signal while allowing DC feedback,
4. Run Simulation: Add a **“.ac dec 10 1 10meg”** command to perform frequency analysis.
5. Plot Loop Gain: After running, plot $V(fb)/V(in)$.

1. Magnitude: $\text{db}(V(\text{fb})/V(\text{in}))$
2. Phase: $\text{ph}(V(\text{fb})/V(\text{in}))$
6. Analyze Phase Margin: The point where the gain is 0dB (magnitude is 1) reveals the phase margin ($180^\circ - |\text{phase}|$)

Key Considerations

- **DC Operating Point:** The DC loop must remain closed. If the feedback is opened, the high open-loop gain will cause the output to rail.
- **Frequency Range:** Sweep from low (e.g., 1Hz) to high (e.g., 100MHz) frequencies to capture the full gain bandwidth.

Links

- Unordered List Item [Omicron Lab Spice Model](#)

From:

<https://wiki.oscardegroot.nl/> - HomeWiki

Permanent link:

<https://wiki.oscardegroot.nl/doku.php?id=computing:ltspice&rev=1777913201>

Last update: 2026/05/04 16:46

