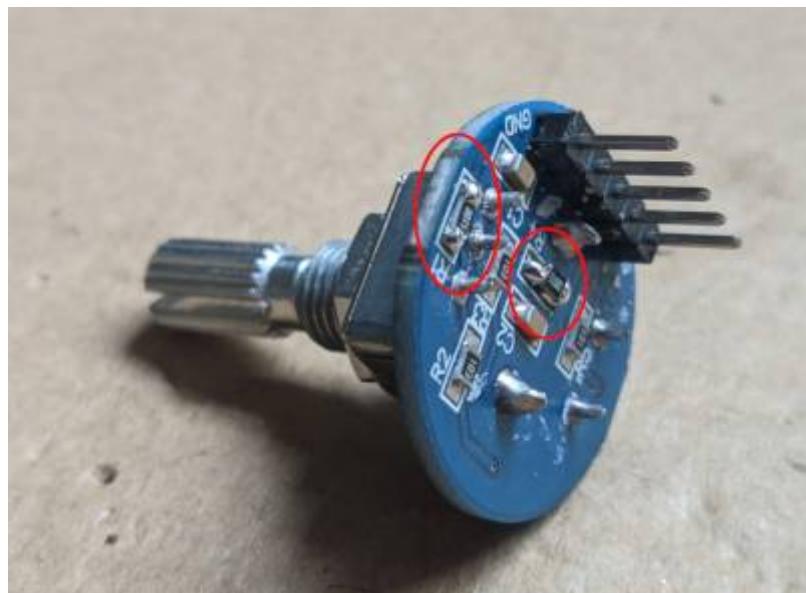


ESP32 - Rotary Encoder

How to reliably read rotary encoder on ESP32?


Background

For usage on my ESP32 projects, I ordered several rotary encoders from Ali Express. It appeared that all of these gave many erratic and unreliable readings. Indicating CW when turning CWW and visa versa. Approximately out of the 20-30 readings was erroneous. Initially I assumed contact bouncing, but the problem persisted after implementing an anti-bounce filter in the software. On a Raspberry this problem does not exist, so it seems that the ESP32 does not work well with this type of rotary encoders. This page describes both cause and solution for this problem.



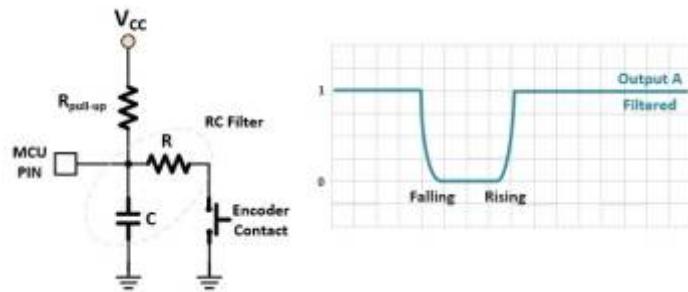Problem cause

It appears that the encoders I bought have RC filters on their output connections. Apparently, with the intention to eliminate contact bounce. However, side effect of this is that the rise and decay times of the rotary pulses do not have sharp edges, but curved edges. The image below is borrowed from www.allaboutcircuits.com (see links below) illustrates this. The ESP32 interrupt mechanism is not able to handle well interrupts and readings on slow edges. This resulted in erroneous readings. E.g. interrupts on negative edges showed a gpio value of 1 in the interrupt routine, where 0 is expected.




Hardware Modifications

The rotary encoders I bought appeared to have resistors of 10k in series with the rotary contact (value of R in picture above). After replacing these resistors to 501 Ohm, the readings improved significantly. The positions for S1 and S2 contacts on the back of the encoder are marked with red circles in the first image.

Method 1

Method 2

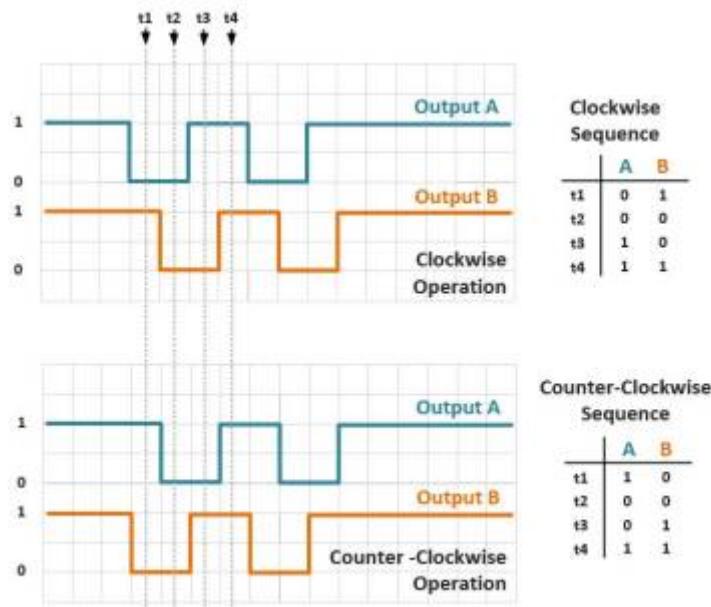

Links

- www.allaboutcircuits.com

From:

<https://wiki.oscardegroot.nl/> - **HomeWiki**

Permanent link:

<https://wiki.oscardegroot.nl/doku.php?id=esp:esp32:esp-idf:rotery-encoder&rev=1728493675>

Last update: **2024/10/09 17:07**

